PowerPC™

Upgrading 66MHz PowerPC 601™ System Designs to the 100MHz PowerPC 601

Application Note AN-PPC-003

Redesign 66MHz PCLK PowerPC 601 systems for use with the 100MHz PowerPC 601 by changing the power supply and clock generation circuits. The upgraded systems offer increased performance and lower power dissipation.

Dale Elson and John Walsh
February 1995

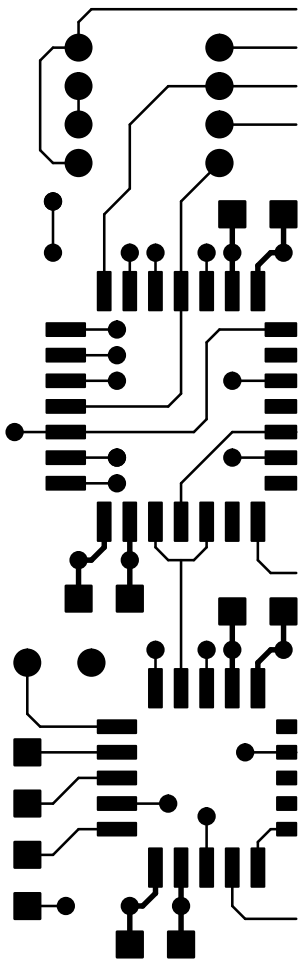

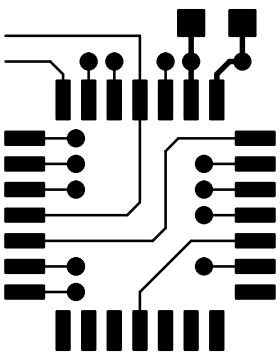

IBM®

PowerPC

Upgrading 66MHz PowerPC 601™ System Designs to the 100MHz PowerPC 601

Dale Elson and John Walsh

Redesign 66MHz PCLK PowerPC 601 systems for use with the 100MHz PowerPC 601 by changing the power supply and clock generation circuits. The upgraded systems offer increased performance and lower power dissipation.

1 Overview

Various PowerPC 601 system designs have been developed for the 66MHz 601. These systems can be upgraded to use the 100MHz PowerPC 601 (the 601v, where the v refers to low voltage) by redesigning the power supply and clock generation circuits. Due to the extent and nature of the required changes, the physical design of the system board will change.

The PowerPC 601 66MHz processor is built in 0.65um CMOS technology. The 601v processor (an exact logical duplicate of the 66MHz PowerPC 601) is built in the higher performance IBM Microelectronics 0.5um CMOS technology. The processors share the same functions, signal I/O, and packages. The typical power dissipation of the 601v at 100MHz is half that of the typical 601 operating at 80Mhz. Other differences between the two processors are the power supply voltages, the power supply pinout, the clock frequencies, and the 2X_PCLK receiver. Some setup and hold times are slightly different. See the PowerPC *601 RISC Microprocessor Hardware Specifications* (IBM document MPR601HSU–03) for details. Some of the following design details refer to the design found in the *PowerPC 601 System Design Kit* (IBM document MPRKITV1–01).

The 601v requires two power supply voltages. The upgraded system design supplies V_{DD} (Vdd_{INT}) = 2.5V for the 601v internal circuits and V_{CC} ($Vdd_{I/O}$) = 5.0V for the 601v I/O circuits.

The clock generation circuit has been changed to supply 2X_PCLK = 200MHz, PCLK_EN# = 100MHz, and BLCK_EN# = 50MHz.

2 Power Supply

In the following discussion the terms V_{CC} and V_{DD} are used in place of $Vdd_{I/O}$ and Vdd_{INT} respectively from the *PowerPC 601 RISC Microprocessor Hardware Specifications*.

2.1 Power Supply Requirements

The 3.6V V_{DD} pins of the 601 have been redefined for the 601v, half of them becoming V_{CC} pins ($V_{CC}1$ through $V_{CC}30$) and half becoming the new V_{DD} pins ($V_{DD}1$ through $V_{DD}29$). The upgraded system design requires V_{DD} = 2.5V ±5% for the 601v internal circuits and V_{CC} = 5.0V ±5% for the 601v I/O circuits. The original 3.6V (3.78V maximum) V_{DD} power supply remains in the design to supply power to the IBM27–82650 Bridge and the clock chip. Processor power dissipation in a typical 601v 100MHz system is 3W less than that of a 601 66MHz system.

2.2 Suggested Power Supply Implementation

The upgraded system design still requires the existing 3.6V V_{DD} regulator, and an additional device is required to supply the new 2.5V V_{DD}. The power element of the new regulator can conveniently be mounted on the opposite side of the existing 3.6V regulator power element heat sink, which is sufficient to cool both of the devices. Refer to Figure 1.0 for circuit details.

The power pins of the 601v have been divided into two groups, neither of which connect to the original 3.6V power supply. $V_{DD}1$ through $V_{DD}29$ are wired to the 2.5V power supply. $V_{CC}1$ through $V_{CC}30$ are wired to the 5.0V power supply. The power plane from the power supplies to the 601v should conform to standard low impedance, high frequency design rules, such as were required for the original V_{DD}.

Note on Figure 1.0 the power pin assignments of the 601v.

Power supply bypass capacitor placement and value selection also follow the same design rules. Note on Figure 1.0 the recommended number and value of the bypass and recharge capacitors, which should be distributed around the 601v according to standard high frequency design rules.

Pullup resistors attached to the 601v CPU bus can be connected to the 3.6V supply to obtain minimum t_{PHL} times. If the timing of the net is not critical and other considerations warrant it, these resistors can be connected to the 5V supply.

3 Clock Circuits

3.1 Clock Circuit Requirements

The logical clock requirements of the 601v are identical to those of the 601. However, to allow for an expected lower amplitude clock signal at 200MHz and beyond, the 2X_PCLK clock receiver has been redesigned with V_{IL}(max) = 0.6V and V_{IH}(min) = 1.8V.

3.2 Suggested Clock Circuit Implementation

The IBM25JP–CLK01 generates 2X_PCLK frequencies up to 132MHz. For 2X_PCLK operation at 200MHz, Motorola offers the MPC970. In the upgraded system design, the 601v runs at 100MHz, with CPU bus operation at 50MHz. This requires 2X_PCLK = 200MHz, PCLK_EN# = 100MHz, and BCLK_EN# = 50MHz.

The MPC970 also provides PCI clocks, which in the design found in the *PowerPC 601 System Design Kit,* are supplied by an AMCC 4403B–66 PCI clock generator. This chip can be removed from the upgraded system design if the designer wishes to use the PCI clocks supplied by the MPC970. Attention to clock skew issues is important to ensure that the clocks meet the skew requirements of the system.

At the desired frequencies, the MPC970 requires either a 25MHz crystal (in x4 mode) or a 12.5MHz crystal (in x8 mode) to generate the 100MHz PCLK_EN#. Figure 2.0 shows the MPC970 with a 12.5MHz crystal in x8 mode.

Figure 2.0 also shows 54.9Ω series termination resistors connected as close as possible to the MPC970. The value of these resistors is chosen to match the output driver impedance to the characteristic impedance of the clock trace. The 10pf capacitors are included to help reduce radiated EMI.

Note that the MPC970 also provides the necessary power management controls to allow the operating system to utilize the 601v power management features. Power management is outside the scope of this application note.

Note that clock design issues are non–trivial. System designers should take care to meet the clock skew and other clock timing requirements of the system. For operational details of the MPC970, refer to the MPC970 data sheet. For board wiring guidelines, refer to the *PowerPC 601 System Design Kit* Volume One, Chapter 6.

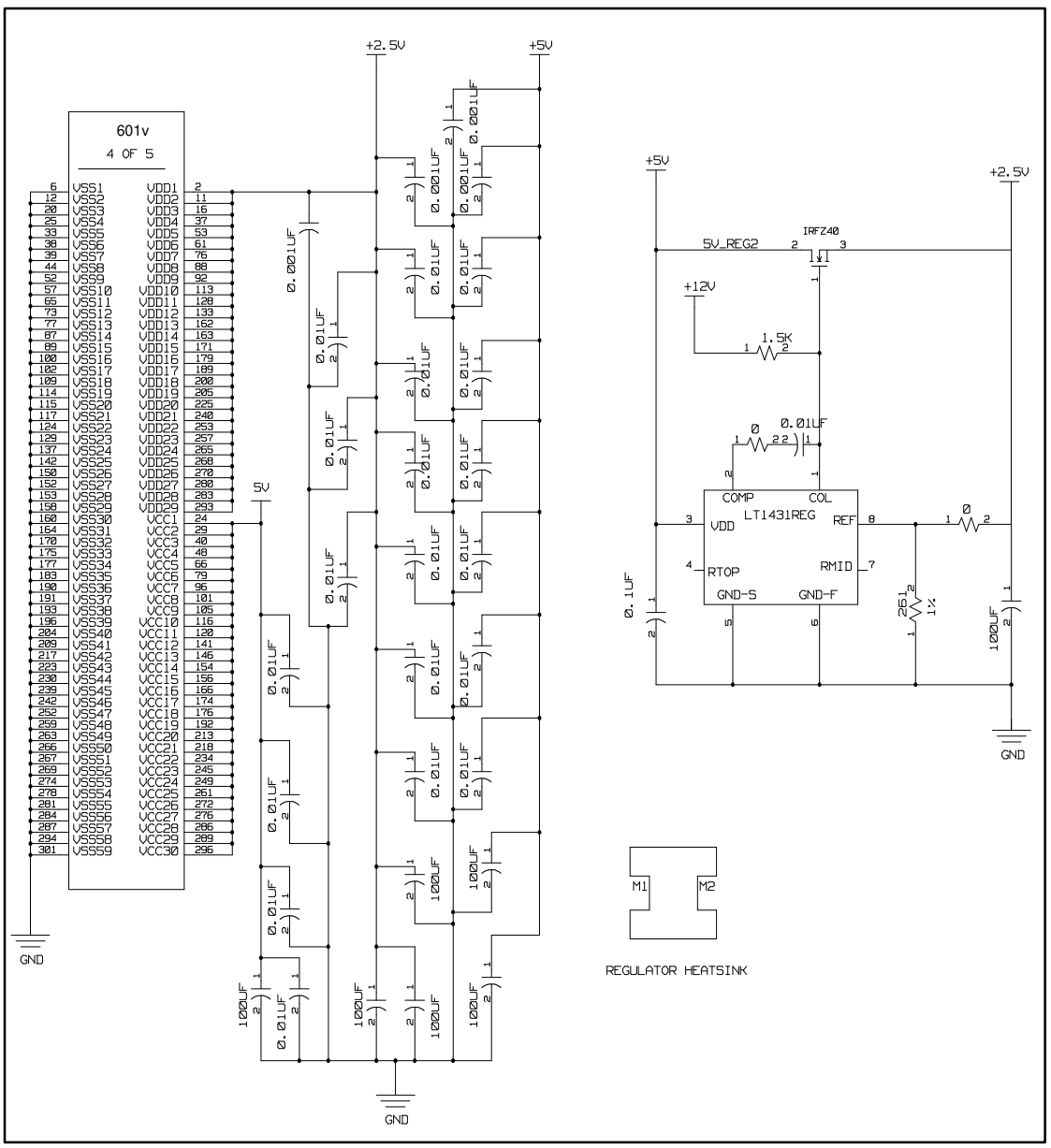
601v
4 OF 5
+2.5V
+5V
5V
GND
0.001UF
0.01UF
100UF
+5V
+2.5V
+12V
5V_REG2
IRFZ40
1.5K
0
0.01UF
COMP
COL
LT1431REG
VDD
REF
RTOP
RMID
GND-S
GND-F
0.1UF
261
1%
100UF
GND
M1
M2
REGULATOR HEATSINK

Figure 1

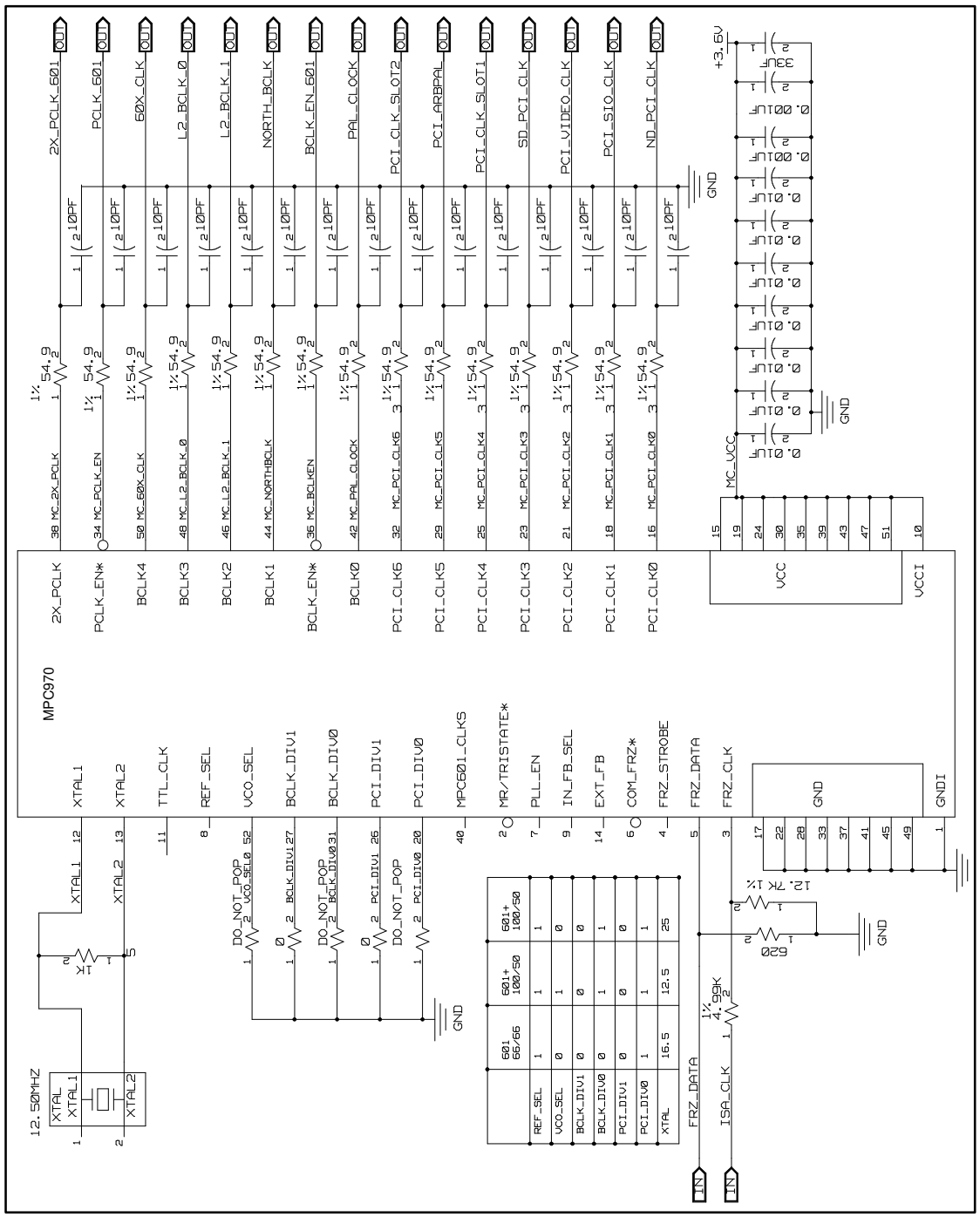
MPC970
12.50MHZ
XTAL
XTAL1
XTAL2
1K
DO_NOT_POP
VCO_SEL0 52
BCLK_DIV1 27
BCLK_DIV0 31
PCI_DIV1 25
PCI_DIV0 20
GND
MPC601_CLKS
MR/TRISTATE*
PLL_EN
IN_FB_SEL
EXT_FB
COM_FRZ*
FRZ_STROBE
FRZ_DATA
FRZ_CLK
ISA_CLK
4.99K
620
12.7K 1%
GNDI
VCCI
VCC
MC_VCC
+3.6V
33UF
0.001UF
0.01UF
2X_PCLK_601
PCLK_601
60X_CLK
L2_BCLK_0
L2_BCLK_1
NORTH_BCLK
BCLK_EN_601
PAL_CLOCK
PCI_CLK_SLOT2
PCI_ARBPAL
PCI_CLK_SLOT1
SD_PCI_CLK
PCI_VIDEO_CLK
PCI_SIO_CLK
ND_PCI_CLK
REF_SEL
VCO_SEL
BCLK_DIV1
BCLK_DIV0
PCI_DIV1
PCI_DIV0
XTAL
601 66/66
601+ 100/50
601+ 100/50
16.5
12.5
25

Figure 2

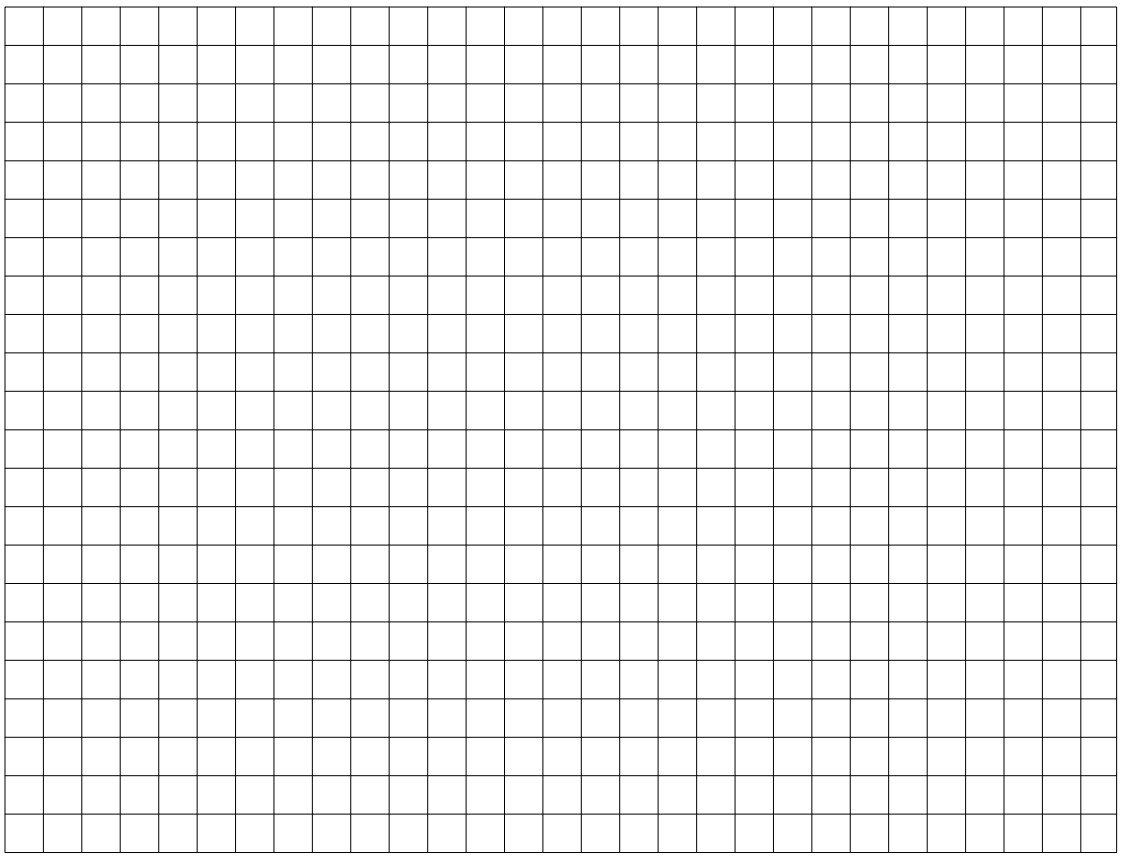

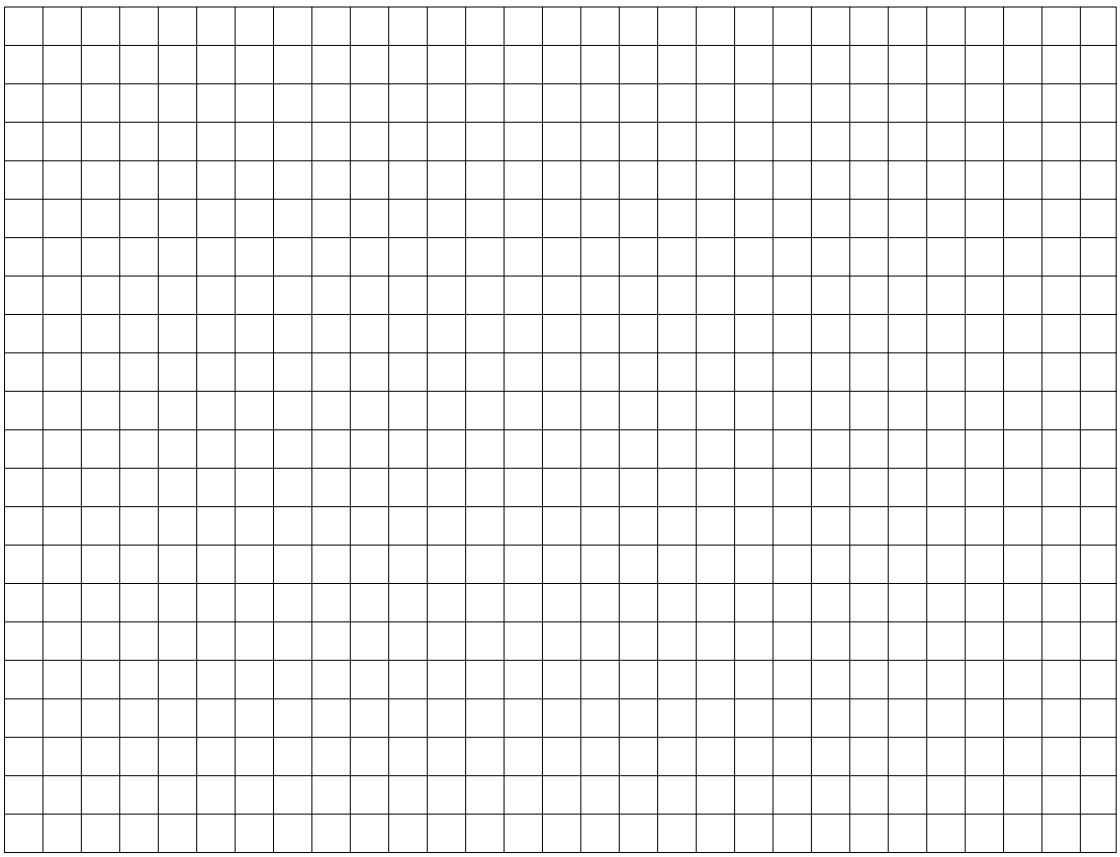

PowerPC

© International Business Machines Corporation, 1995. Printed in the United States of America 2/95. All Rights reserved.

IBM Microelectronics, PowerPC, PowerPC 601, PowerPC 603, PowerPC 604, RiscWatch, and AIX are trademarks of the IBM corporation. IBM and the IBM logo are registered trademarks of the IBM corporation. Other company names and product identifiers are trademarks of the respective companies.

This document contains information which is subject to change by IBM without notice. IBM assumes no responsibility or liability for any use of the information contained herein. Nothing in this document shall operate as an express or implied license or indemnity under the intellectual property rights of IBM or third parties. The products described in this document are not intended for use in implantation or other direct life-support applications where malfunction may result in physical harm or injury to persons. NO WARRANTIES OF ANY KIND, INCLUDING BUT NOT LIMITED TO, THE IMPLIED WARRANTIES OF MERCHANTABILITY OR FITNESS FOR A PARTICULAR PURPOSE, ARE OFFERED IN THIS DOCUMENT.

USA and Canada:
IBM Microelectronics Division
1580 Route 52, Bldg. 504
Hopewell Junction, NY 12533-6531
Tel: (800) PowerPC
Fax: (800) PowerFax

Europe:
IBM
La Pompignane BP 1021
34006 Montpellier, France
Tel: (33) 6713–5757 (Français)
(33) 6713–5756 (Italiano)
Fax: (33) 6713–5750
(from Paris add 16)

Europe:
IBM
Informations Systeme GmbH
Laatzener Str. 1
30539 Hannover, Germany
Tel: (49) 511–516–3444 (English)
(49) 511–516–3555 (Deutsche)
Fax: (49) 511–516–3888

Japan:
IBM
800, Ichimiyake
Yasu–cho, Yasu–gun
Shiga–ken, Japan 520–23
Tel: (81) 775–87–4745
Fax: (81) 775–87–4735

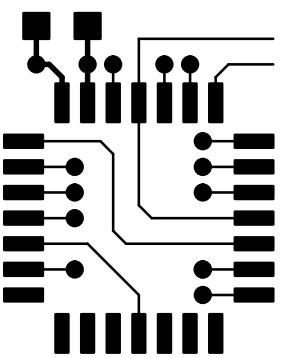

Document Number: MPRA03APU–01